

I-V Characteristics of a diode

Chirag Verma

Enrollment Number : 21615007

September 26, 2021

1 Aim

- To study I-V characteristics of a p-n junction diode (Si/ Ge).
- Also, to Find: Dynamic and Static Resistance of the Si Diode used.

2 Apparatus Required

p-n junction diode, voltmeter, micro/mili-ammeter, resistance, DC voltage source

3 Diagram

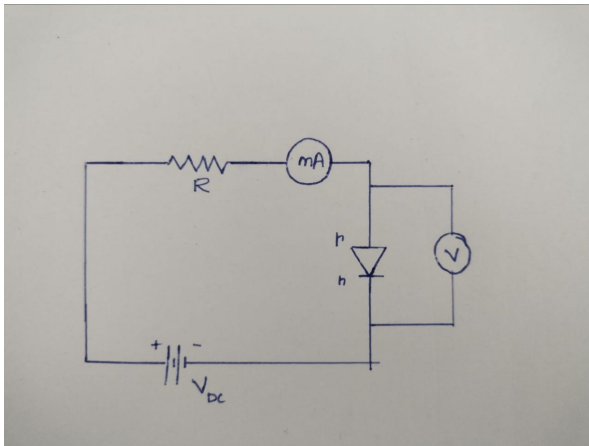


Figure 1: forward biased

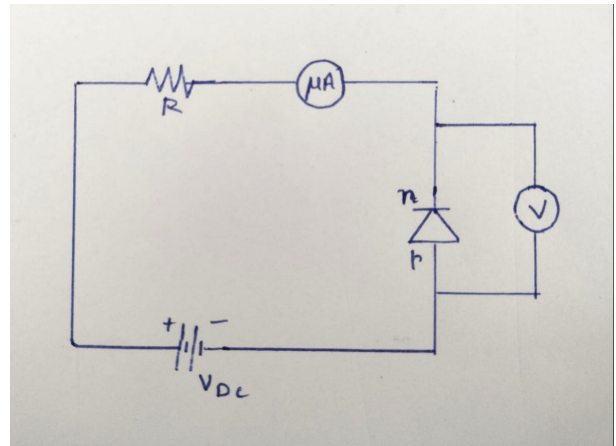


Figure 2: reverse biased

4 Formula Used

4.1 Diode Equation

$$I_f = I_s \left(\exp \left(\frac{V_f}{\eta \left(\frac{kT}{q} \right)} \right) - 1 \right) \quad (1)$$

where

$I_s \equiv$ reverse saturation current, $I_f \equiv$ forward current, $V_f \equiv$ forward voltage,
 $V_T = \frac{kT}{q} \equiv$ thermal voltage, $k \equiv$ Boltzmann constant, $T \equiv$ absolute temperature,
 $q \equiv$ electronic charge

4.2 Static Resistance

$$r_s = \frac{V_{dQ}}{I_{dQ}} \quad (2)$$

i.e. it is defined as the ratio of the voltage across the diode to the current flowing through the diode.

In reverse bias, $r_s \gg 1$.

4.3 Dynamic Resistance

$$r_d = \frac{\Delta V}{\Delta I} \quad (3)$$

i.e. it is defined as the ration of the change in voltage across the diode for some corresponding change in the current flowing through the diode. Used, generally, in AC analysis.

5 Theory

5.1 Forward Bias

Positive terminal of the battery is connected with the p side, and the negative terminal is connected with the n side of the diode. Due to the applied voltage (and the drift current), the width of the depletion region starts decreasing. Hence, a forward current starts flowing through the diode.

In an ideal case, the diode acts as a closed switch.

For Silicon, the cut-in/knee voltage is 0.6V.

For Germanium, the cut-in/knee voltage is 0.3V.

5.2 Reverse Bias

Positive terminal of the battery is connected with the n side, and the negative terminal is connected with the p side of the diode. Due to this biasing, very little or no current flows through the diode until Zener/Avalanche breakdown occurs. This can also be explained by the increase in the width of the depletion region.

In an ideal case, the diode acts as an open switch.

6 Observations and Plots, and Static Resistances

6.1 Silicon Diode IN4001

- Forward Bias

1. Resistance, $R = 100\Omega$

| S.No. | V_{dc} | $V_f(V)$ | $I_f(mA)$ | Static Resistance ($\times 10^3\Omega$) |
|-------|----------|----------|-----------|---|
| 01 | 0 | 0 | 0 | N.A. |
| 02 | 0.7 | 0.589 | 0.997 | 0.5907 |
| 03 | 0.8 | 0.593 | 1.99 | 0.2979 |
| 04 | 0.9 | 0.596 | 2.99 | 0.1993 |
| 05 | 1.0 | 0.599 | 3.99 | 0.1501 |
| 06 | 1.1 | 0.601 | 4.99 | 0.1204 |
| 07 | 1.2 | 0.603 | 5.98 | 0.1000 |
| 08 | 1.3 | 0.605 | 6.98 | 0.0866 |
| 09 | 1.4 | 0.607 | 7.98 | 0.0760 |
| 10 | 1.5 | 0.609 | 8.97 | 0.0678 |
| 11 | 1.6 | 0.611 | 9.97 | 0.0612 |
| 12 | 1.7 | 0.612 | 11.0 | 0.0556 |
| 13 | 1.8 | 0.614 | 12.0 | 0.0511 |
| 14 | 1.9 | 0.615 | 13.0 | 0.0473 |
| 15 | 2.0 | 0.617 | 14.0 | 0.0440 |
| 16 | 2.2 | 0.619 | 16.0 | 0.0386 |
| 17 | 2.4 | 0.621 | 17.9 | 0.0349 |
| 18 | 2.6 | 0.624 | 19.9 | 0.03134 |
| 19 | 2.8 | 0.625 | 21.9 | 0.0285 |
| 20 | 3.0 | 0.627 | 23.9 | 0.026 |
| 21 | 3.2 | 0.629 | 25.9 | 0.0242 |
| 22 | 3.4 | 0.630 | 27.9 | 0.0225 |
| 23 | 3.6 | 0.632 | 29.9 | 0.0211 |
| 24 | 3.8 | 0.633 | 31.9 | 0.0198 |
| 25 | 4.0 | 0.635 | 33.9 | 0.0187 |
| 26 | 4.2 | 0.636 | 35.9 | 0.0177 |
| 27 | 4.4 | 0.637 | 37.9 | 0.0168 |
| 28 | 4.6 | 0.638 | 39.9 | 0.0159 |
| 29 | 4.8 | 0.639 | 41.9 | 0.0152 |
| 30 | 5.0 | 0.641 | 43.9 | 0.014 |

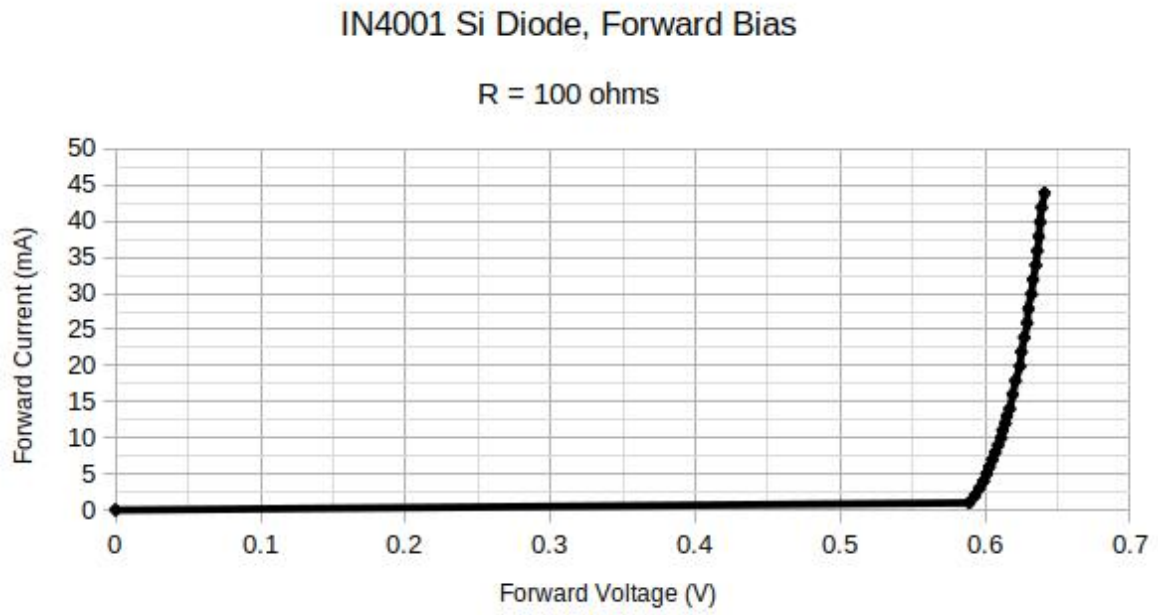


Figure 3: IN4001 Si Diode, Forward Bias, R = 100Ω

2. Resistance, R = 500Ω

| S.No. | V_{dc} | $V_f(V)$ | $I_f(mA)$ | Static Resistance ($\times 10^3 \Omega$) |
|-------|----------|----------|-----------|--|
| 01 | 0 | 0 | 0 | N.A |
| 02 | 0.2 | 0 | 0 | N.A |
| 03 | 0.7 | 0.548 | 0.200 | 2.74 |
| 04 | 1.0 | 0.557 | 0.800 | 0.696 |
| 05 | 1.3 | 0.564 | 1.40 | 0.4028 |
| 06 | 1.6 | 0.569 | 2.00 | 0.2845 |
| 07 | 1.9 | 0.574 | 2.60 | 0.2207 |
| 08 | 2.2 | 0.577 | 3.20 | 0.1803 |
| 09 | 2.5 | 0.581 | 3.80 | 0.2075 |
| 10 | 2.8 | 0.584 | 4.40 | 0.1332 |
| 11 | 3.1 | 0.586 | 5.00 | 0.117 |
| 12 | 3.4 | 0.598 | 5.60 | 0.1051 |
| 13 | 3.7 | 0.591 | 6.20 | 0.0953 |
| 14 | 4.0 | 0.593 | 6.80 | 0.0872 |
| 15 | 4.3 | 0.595 | 7.40 | 0.074625 |
| 16 | 4.6 | 0.597 | 8.00 | 0.0745 |
| 17 | 4.9 | 0.598 | 8.59 | 0.069 |

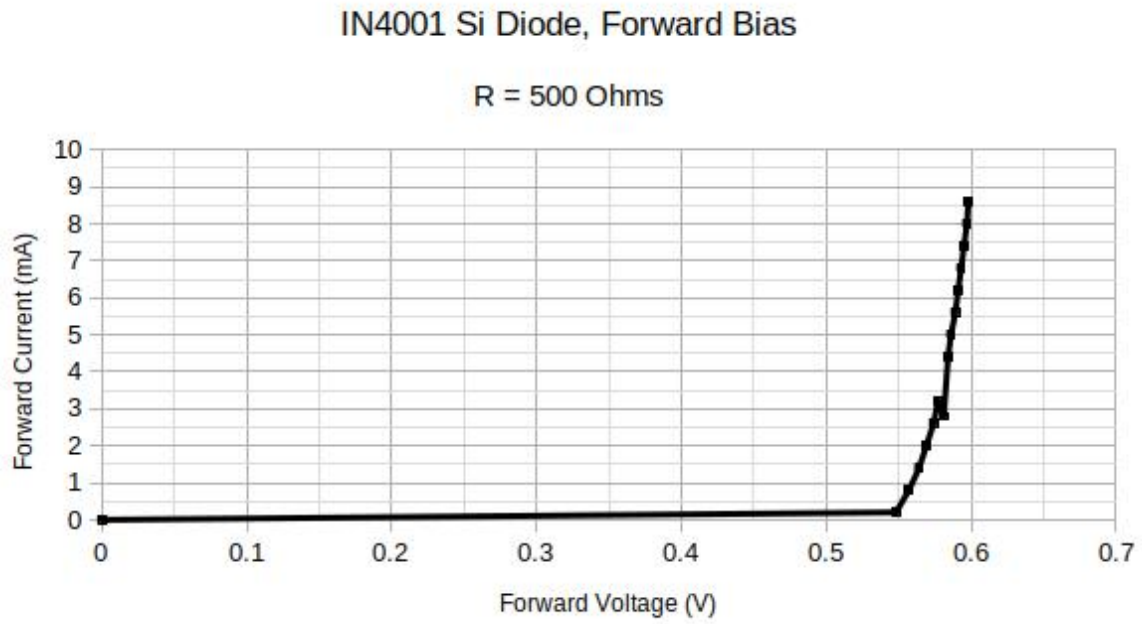


Figure 4: IN4001 Si Diode, Forward Bias, $R = 500\Omega$

3. Resistance, $R = 2000\Omega$

| S.No. | V_{dc} | $V_f(V)$ | $I_f(mA)$ | Static Resistance ($\times 10^3\Omega$) |
|-------|----------|----------|-----------|---|
| 01 | 0 | 0 | 0 | N.A. |
| 02 | 0.2 | 0 | 0 | N.A. |
| 03 | 0.7 | 0.512 | 0.05 | 10.24 |
| 04 | 1.0 | 0.521 | 0.20 | 2.605 |
| 05 | 1.3 | 0.528 | 0.35 | 1.508 |
| 06 | 1.6 | 0.533 | 0.50 | 1.066 |
| 07 | 1.9 | 0.537 | 0.650 | 0.826 |
| 08 | 2.2 | 0.541 | 0.80 | 0.6726 |
| 09 | 2.5 | 0.545 | 0.950 | 0.573 |
| 10 | 2.8 | 0.548 | 1.10 | 0.498 |
| 11 | 3.1 | 0.550 | 1.25 | 0.44 |
| 12 | 3.4 | 0.553 | 1.40 | 0.395 |
| 13 | 3.7 | 0.555 | 1.55 | 0.358 |
| 14 | 4.0 | 0.557 | 1.70 | 0.327 |
| 15 | 4.3 | 0.559 | 1.85 | 0.302 |
| 16 | 4.6 | 0.560 | 2.00 | 0.28 |
| 17 | 4.9 | 0.562 | 2.15 | 0.2613 |

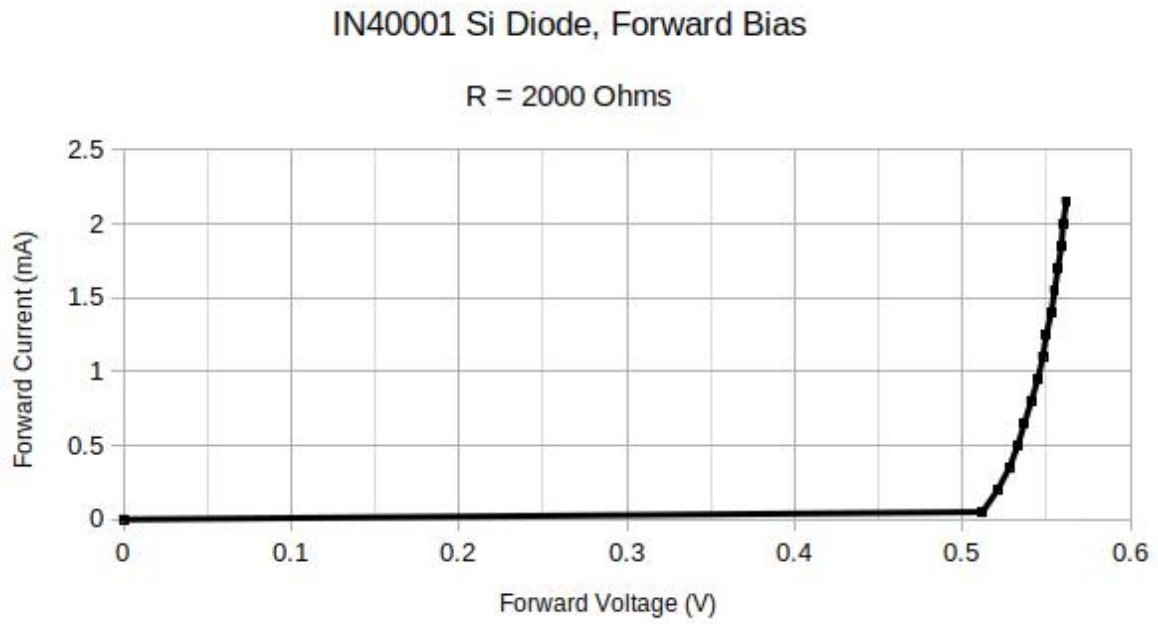


Figure 5: IN4001 Si Diode, Forward Bias, $R = 2000\Omega$

- Reverse Bias
Resistance, $R = 100\Omega$

| S.No. | V_{dc} | $V_r(V)$ | $I_r(\mu A)$ | Static Resistance ($\times 10^6\Omega$) |
|-------|----------|----------|--------------|---|
| 01 | 0.2 | 0.170 | 0.100 | 1.7 |
| 02 | 0.35 | 303 | 0.100 | 3.03 |
| 03 | 0.50 | 0.439 | 0.100 | 4.39 |
| 04 | 0.90 | 0.807 | 0.100 | 8.07 |
| 05 | 1.5 | 1.37 | 0.100 | 13.7 |
| 06 | 2.0 | 1.84 | 0.100 | 18.4 |
| 07 | 3.0 | 2.80 | 0.100 | 28 |
| 08 | 4.0 | 3.77 | 0.100 | 37.7 |
| 09 | 6.0 | 5.73 | 0.100 | 57.3 |
| 10 | 8.0 | 5.52 | 0.100 | 77.2 |
| 11 | 10.0 | 9.71 | 0.100 | 97.1 |
| 12 | 15.0 | 14.8 | 0.100 | 148 |
| 13 | 20.0 | 19.9 | 0.100 | 199 |
| 14 | 25.0 | 25.0 | 0.100 | 250 |
| 15 | 29.0 | 29.1 | 0.100 | 291 |
| 16 | 30.0 | 30.2 | 75.00 | — |
| 17 | 30.1 | 30.3 | 75.25 | — |
| 18 | 30.15 | 30.3 | 75.37 | — |
| 19 | 30.2 | 30.4 | 75.50 | — |

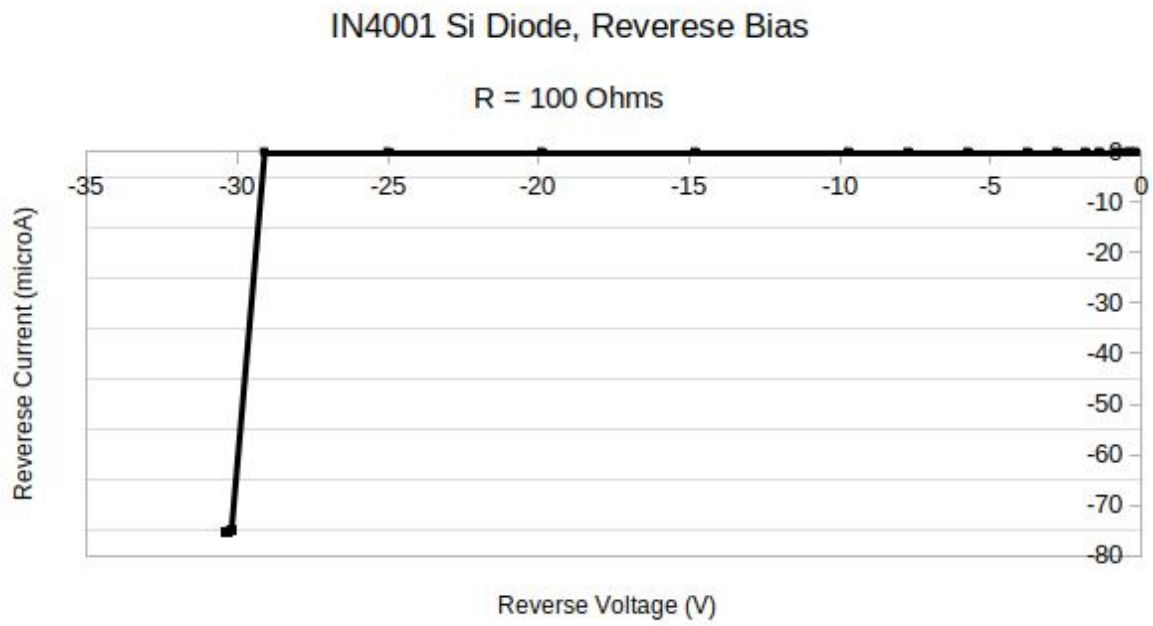


Figure 6: IN4001 Si Diode, Reverse Bias, $R = 100\Omega$

6.2 Germanium Diode

- Forward Bias
Resistance, $R = 1000\Omega$

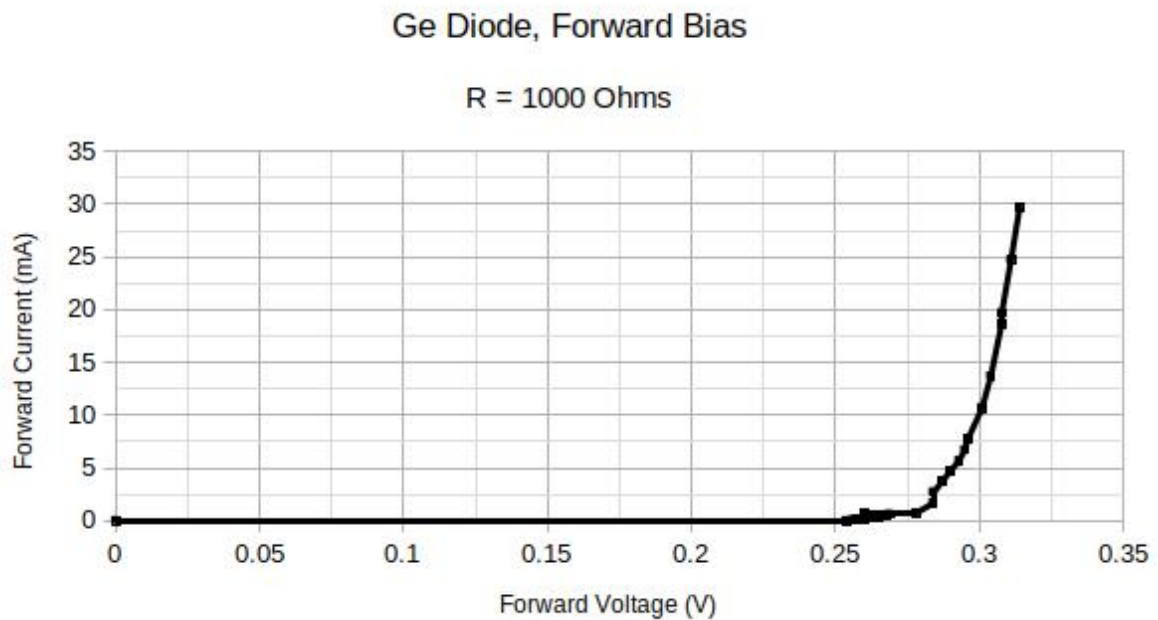


Figure 7: Ge Diode, Forward Bias, $R = 1000\Omega$

| S.No. | V_{dc} | $V_f(V)$ | $I_f(mA)$ | Static Resistance ($\times 10^3 \Omega$) |
|-------|----------|----------|-----------|--|
| 01 | 0 | 0 | 0 | N.A. |
| 02 | 0.2 | 0 | 0 | N.A. |
| 03 | 0.3 | 0.254 | 0 | 5.12 |
| 04 | 0.35 | 0.256 | 0.050 | 2.57 |
| 05 | 0.4 | 0.257 | 0.100 | 1.72 |
| 06 | 0.45 | 0.259 | 0.150 | 1.3 |
| 07 | 0.50 | 0.260 | 0.200 | 1.048 |
| 08 | 0.55 | 0.262 | 0.250 | 0.876 |
| 09 | 0.60 | 0.263 | 0.300 | 0.754 |
| 10 | 0.65 | 0.264 | 0.350 | 0.662 |
| 11 | 0.70 | 0.265 | 0.400 | 0.5911 |
| 12 | 0.75 | 0.266 | 0.450 | 0.534 |
| 13 | 0.80 | 0.267 | 0.500 | 0.487 |
| 14 | 0.85 | 0.267 | 0.550 | 0.448 |
| 15 | 0.90 | 0.268 | 0.600 | 0.4 |
| 16 | 0.95 | 0.269 | 0.650 | 0.397 |
| 17 | 1.00 | 0.278 | 0.700 | 0.167 |
| 18 | 2.00 | 0.284 | 1.70 | 0.105 |
| 19 | 3.00 | 0.287 | 2.70 | 0.077 |
| 20 | 4.00 | 0.290 | 3.70 | 0.061 |
| 21 | 5.00 | 0.293 | 4.70 | 0.051 |
| 22 | 6.00 | 0.295 | 5.70 | 0.044 |
| 23 | 7.00 | 0.296 | 6.70 | 0.038 |
| 24 | 8.00 | 0.301 | 7.70 | 0.028 |
| 25 | 11.00 | 0.304 | 10.70 | 0.022 |
| 26 | 14.00 | 0.308 | 13.70 | 0.016 |
| 27 | 19.00 | 0.308 | 18.70 | 0.015 |
| 28 | 20.00 | 0.311 | 19.70 | 0.0125 |
| 29 | 25.00 | 0.314 | 24.70 | 0.011 |
| 30 | 30.00 | 0.641 | 29.70 | 0.0105 |

- Reverse Bias
Resistance, $R = 1000\Omega$

| S.No. | V_{dc} | $V_r(V)$ | $I_r(mA)$ | Static Resistance ($\times 10^3 \Omega$) |
|-------|----------|----------|-----------|--|
| 01 | 0.2 | 0.2 | 0 | N.A. |
| 02 | 0.25 | 0.25 | 0 | N.A. |
| 03 | 0.3 | 0.3 | 0 | N.A. |
| 04 | 2 | 2.0 | 0 | N.A. |
| 05 | 3 | 3.0 | 0 | N.A. |
| 06 | 4 | 4.0 | 0 | N.A. |
| 07 | 10 | 10.0 | 0 | N.A. |
| 08 | 20 | 20.0 | 0 | N.A. |
| 09 | 29.95 | 29.9 | 0 | N.A. |
| 10 | 30 | 30.0 | 30 | — |
| 11 | 30.05 | 30.1 | 30.05 | — |
| 12 | 30.1 | 30.1 | 30.10 | — |
| 13 | 30.15 | 30.1 | 30.15 | — |
| 14 | 30.2 | 30.2 | 30.19 | — |

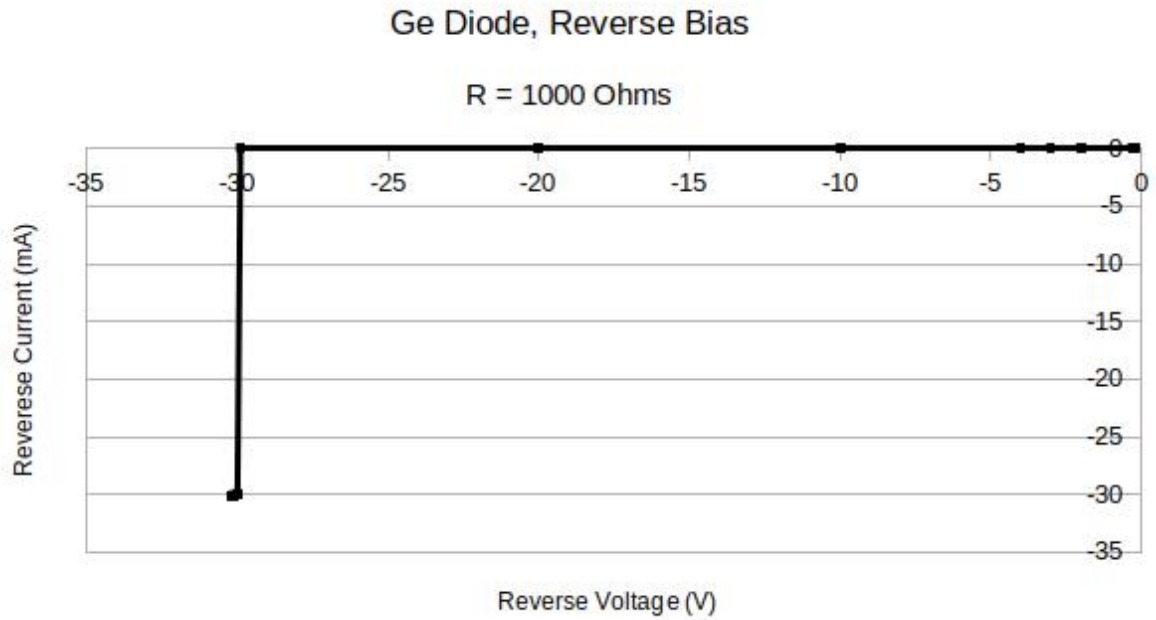


Figure 8: Ge Diode, Reverse Bias, $R = 1000\Omega$

7 Analysis

The static resistances have been calculated for specific diode currents in the previous section (tables). Dynamic resistances haven't been calculated since they are usually used in AC circuits (and the circuit in the simulator was a DC one).